

Expt No: 8  
December 2021

Date:4

## Latches and Flip flops


### Objective

- To study and realize the given latches and flip-flops using Tinkercad.

### Lab Experiments:


1. Use Tinkercad to verify the truth table for basic SR Latch using NAND gate.

#### *Circuit Diagram*

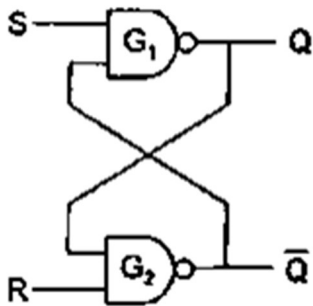


#### *Truth table*

<i>S</i>	<i>R</i>	<i>Q</i>	<i>Q'</i>
0	0	X	X
0	1	1	0
1	0	0	1
1	1	<i>Q</i>	<i>Q'</i>

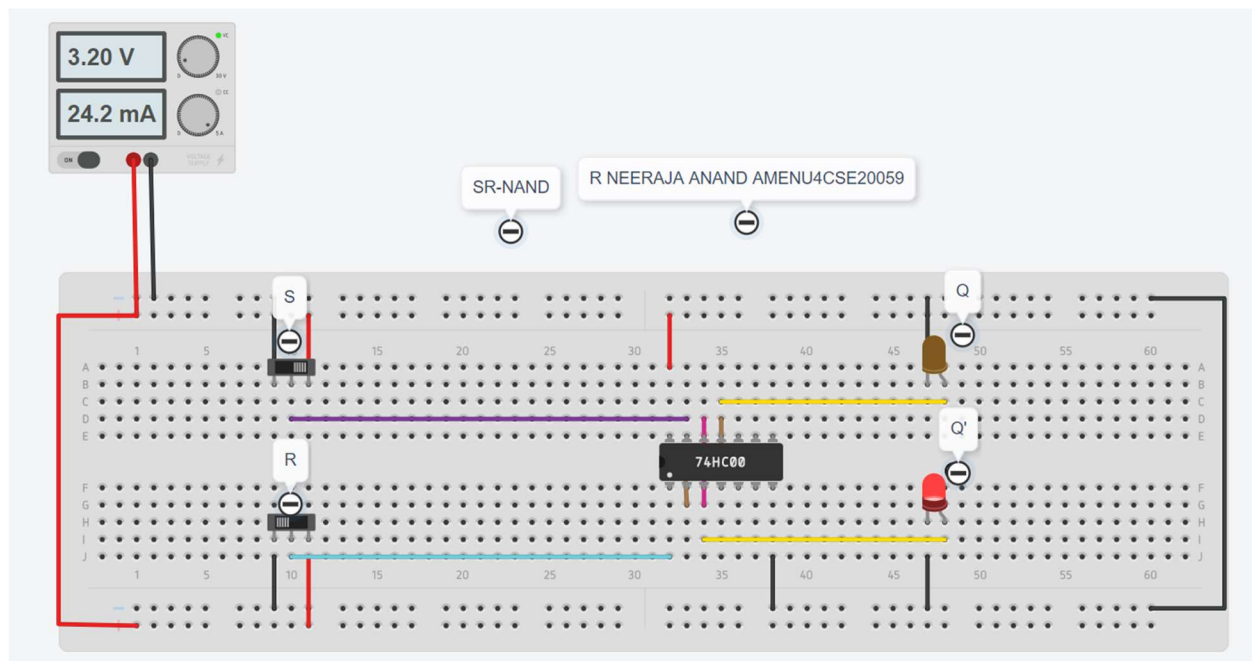**Simulation diagram**

2. Use Tinkercad to verify the Characteristic tables for D flip flop.

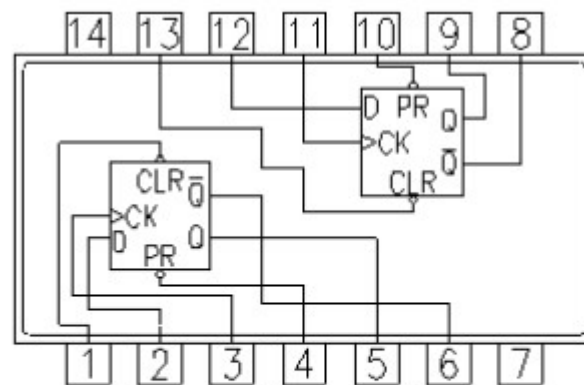**Pin layout**


7474

Dual D Flip-Flop  
with Preset and Clear




3. Use Tinkercad to verify the Characteristic tables for JK flip flop.

### Pin layout

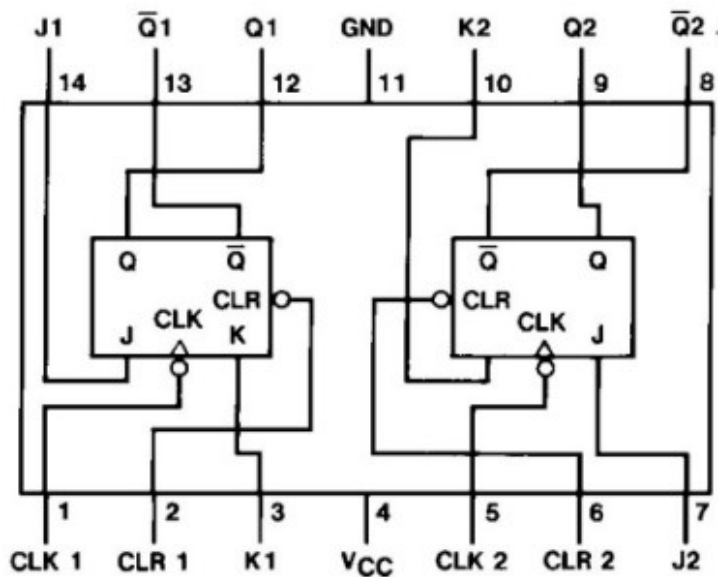

### Truth table

J	K	CLK	Q
0	0	High	Q0 No change
1	0	High	1
0	1	High	0
1	1	high	Q0'

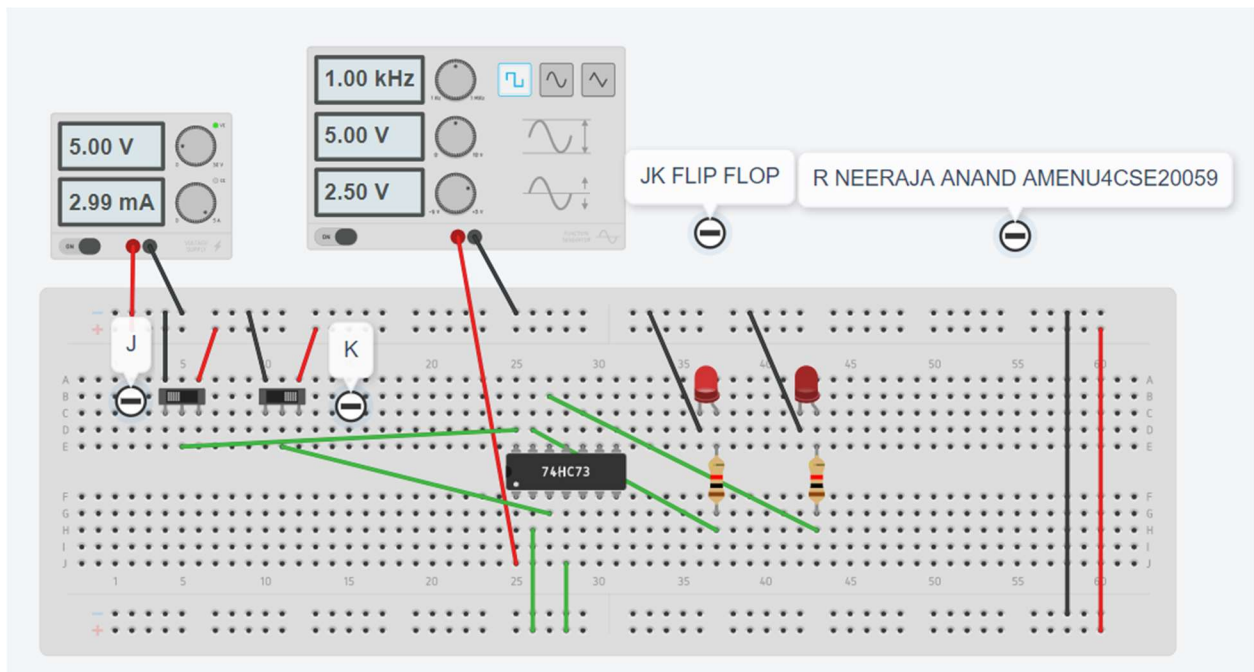**Simulation diagram**

- **Result:** Studied and realized the given latches and flip-flops using Tinkercad.

Name: R Neeraja Anand

Roll: AMENU4CSE20059